
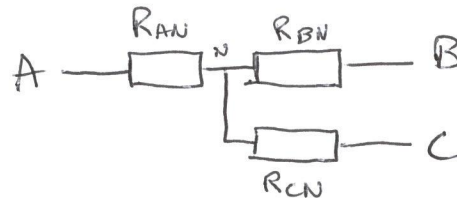
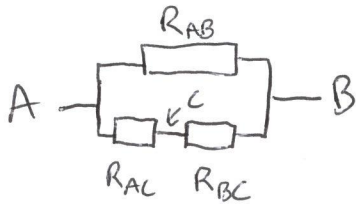
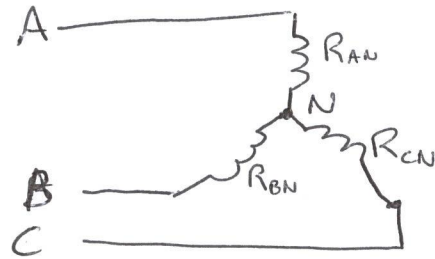


①

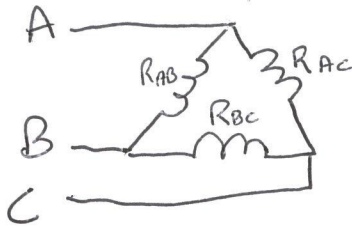



$$R_{AB} = R_{AC} = R_{BC} = R_{\Delta}$$

$$R_{AN} = R_{BN} = R_{CN} = R_{*}$$

$$\begin{aligned} R_T &= R_{AB} // (R_{AC} + R_{BC}) \\ &= R_{\Delta} // 2R_{\Delta} \\ &= \frac{R_{\Delta} \cdot 2R_{\Delta}}{3R_{\Delta}} = \frac{2}{3} R_{\Delta} \end{aligned}$$

$$\begin{aligned} R_T &= R_{AN} + R_{BN} \\ &= R_{*} + R_{*} \\ &= 2R_{*} \end{aligned}$$

Now short B to C

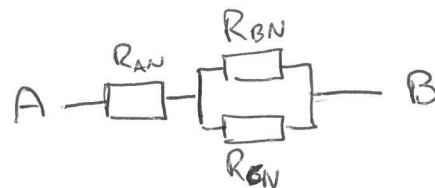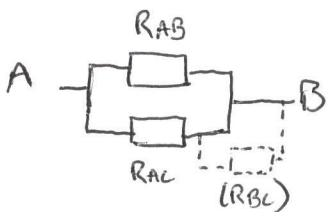

$$\begin{aligned} R_{T(\text{short})} &= R_{AB} // R_{AC} \\ &= R_{\Delta} // R_{\Delta} \\ &= \frac{R_{\Delta} \cdot R_{\Delta}}{2R_{\Delta}} = \frac{1}{2} R_{\Delta} \end{aligned}$$

$$\begin{aligned} R_{T(\text{short})} &= R_{AN} + R_{BN} // R_{CN} \\ &= R_{*} + (R_{*} // R_{*}) \\ &= \frac{3R_{*}}{2} \end{aligned}$$


(2)

Using a rheostat, 2 legs of a potentiometer, or a long bit of wire, make a resistor the same resistance as  $R_T(\text{short})$  i.e. the same resistance as you measured whilst 2 of the terminals were shorted. Call this  $R_S$

So if it's a  $\Delta$ ,  $R_S = \frac{1}{2} R_\Delta$

if it's a  $*$ ,  $R_S = \frac{3}{2} R_*$

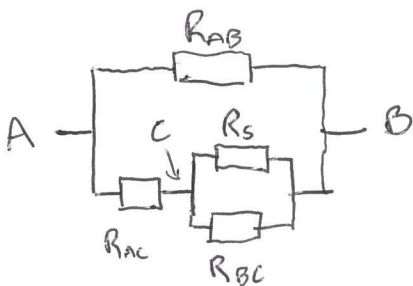
Replace the short between B and C with  $R_S$ :



$$R_{AB} = R_{AC} = R_{BC} = R_\Delta$$

$$R_S = \frac{R_\Delta}{2}$$
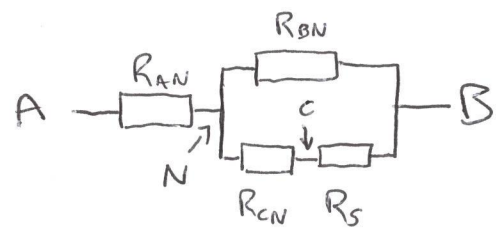
$$\begin{aligned} R_{T(R_S)} &= R_\Delta // \left[ R_\Delta + \left( R_\Delta // \frac{R_\Delta}{2} \right) \right] \\ &= R_\Delta // \left[ R_\Delta + R_\Delta / 3 \right] \\ &= R_\Delta // \frac{4R_\Delta}{3} \\ &= \frac{7R_\Delta}{4} \end{aligned}$$



$$R_{AN} = R_{BN} = R_{CN} = R_*$$

$$R_S = \frac{3R_*}{2}$$

$$\begin{aligned} R_{T(R_S)} &= R_* + \left[ R_* // \left( R_* + \frac{3R_*}{2} \right) \right] \\ &= R_* + \left[ R_* // \frac{5R_*}{2} \right] \\ &= R_* + \frac{3R_*}{7} \\ &= \frac{12R_*}{7} \end{aligned}$$

Your ratio of  $\frac{R_s}{R_T(R_s)}$  tells you whether it's

\* or  $\Delta$  :



$$\frac{R_s}{R_T(R_s)} = \frac{R_{\Delta}/2}{7R_{\Delta}/4}$$

$$= \frac{1}{2} \times \frac{4}{7}$$

$$\therefore \frac{R_s}{R_T(R_s)} = \frac{2}{7}$$



$$\frac{R_s}{R_T(R_s)} = \frac{3R^*/2}{12R^*/7}$$

$$= \frac{3}{2} \times \frac{7}{12}$$

$$= \frac{21}{24}$$

$$\therefore \frac{R_s}{R_T(R_s)} = \frac{7}{8}$$

Now you know whether it's  $\Delta$  or \*, you can work out  $R_{\Delta}$  or  $R^*$  :



$$R_s = R_{\Delta}/2$$

$$\therefore R_{\Delta} = 2R_s$$



$$R_s = \frac{3R^*}{2}$$

$$\therefore R^* = \frac{2R_s}{3}$$

Steve