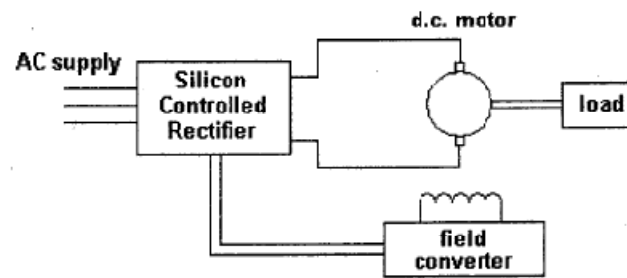


Question 12 Fig Q12 shows an electronic method of speed control of a d.c. motor. With reference to the diagram, explain the principle of operation and how the system operates.



Solid State Speed Control of d.c. Motor

Fig Q12